

Op Amps and RC Filters

Analog Electronics, 2026-04-03


Resistance and RC Time Constant Problems from Grisha

1. Both Series and Parallel Resistors in the Same Circuit!!

Hint: First collapse the two $3\text{k}\Omega$ resistors that are in parallel into a single equivalent resistor using

$$R_{\text{equivalent}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

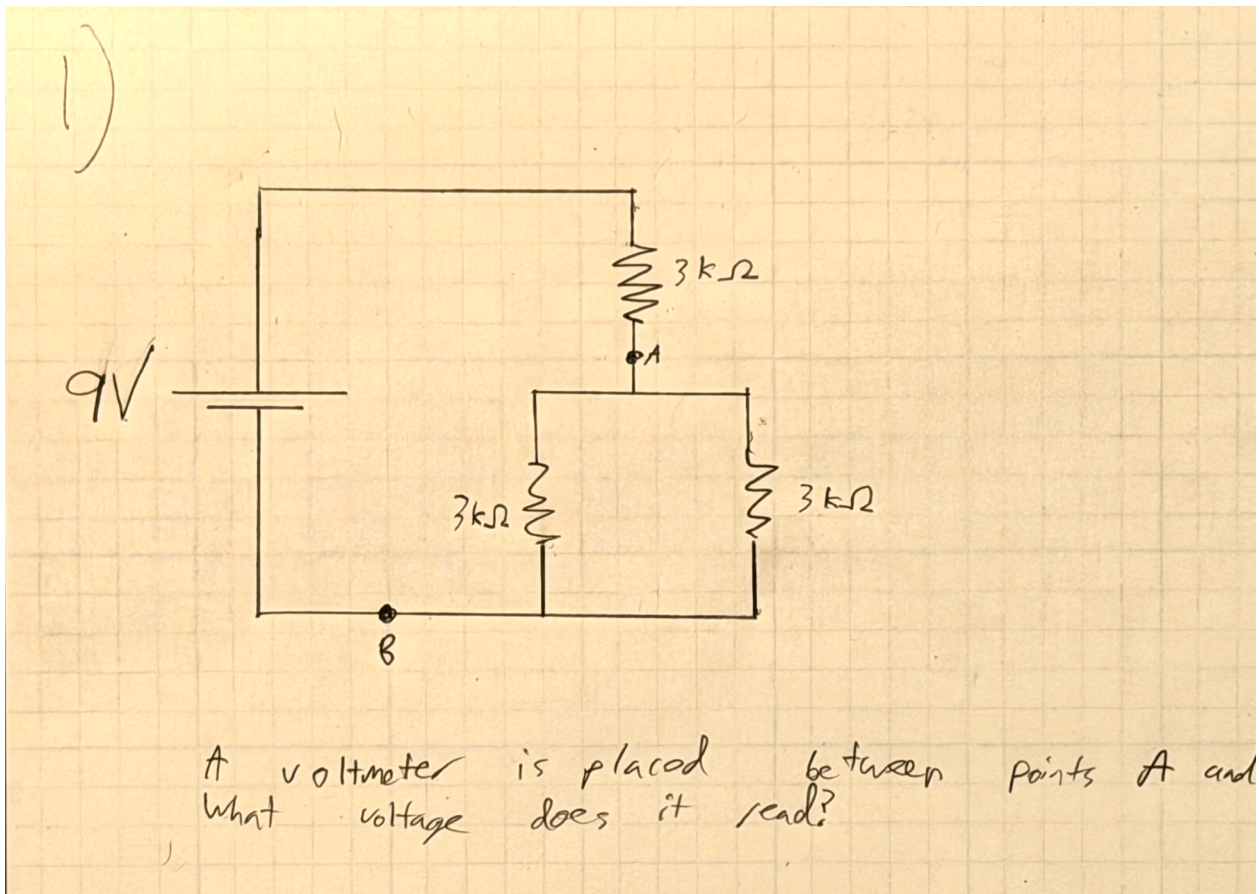
You should get something smaller than either R_1 or R_2 . Now that it is collapsed into a single equivalent resistor, you have an ordinary voltage divider problem.



2. RC Time Constants — These are Tricky!! Don't stress if you can't do (b), (c), and (d).

Do (a) before looking at the hint/discussion below.

2)

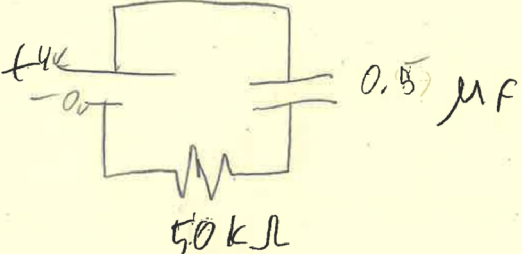

50 k Ω 0.5 μ F

d) how many times per second can the capacitor charge from 1V to 3V and then discharge to 1V.

2.a) what is the RC time constant for this circuit?

b) how long does it take for the capacitor to charge to 2V

c) how long does it take to get the capacitor from 1V to 3V?

HINT/DISCUSSION ON (b), (c), and (d):

You can make rough estimates by putting $T = RC$ into the exact answer,


$$V(t) = V_0(1 - e^{-t/T}),$$

and then graphing it. On the facing page is a graph that is sufficiently detailed, that you should be able to read off the times to the nearest thousandth or so of a second.

For part (d) you just take the inverse of the time to go from 1V to 3V and you have the number of times per second that can happen. Then divide by 2, to account for both charge and discharge.


```
In[23]:= spacings = {Range[0.000, 0.040, 0.002], Automatic};  
f[t_] := 4 (1 - Exp[-t / T]);  
Plot[f[t], {t, 0.0, 0.04}, Ticks → spacings, GridLines → spacings]
```

Out[25]=

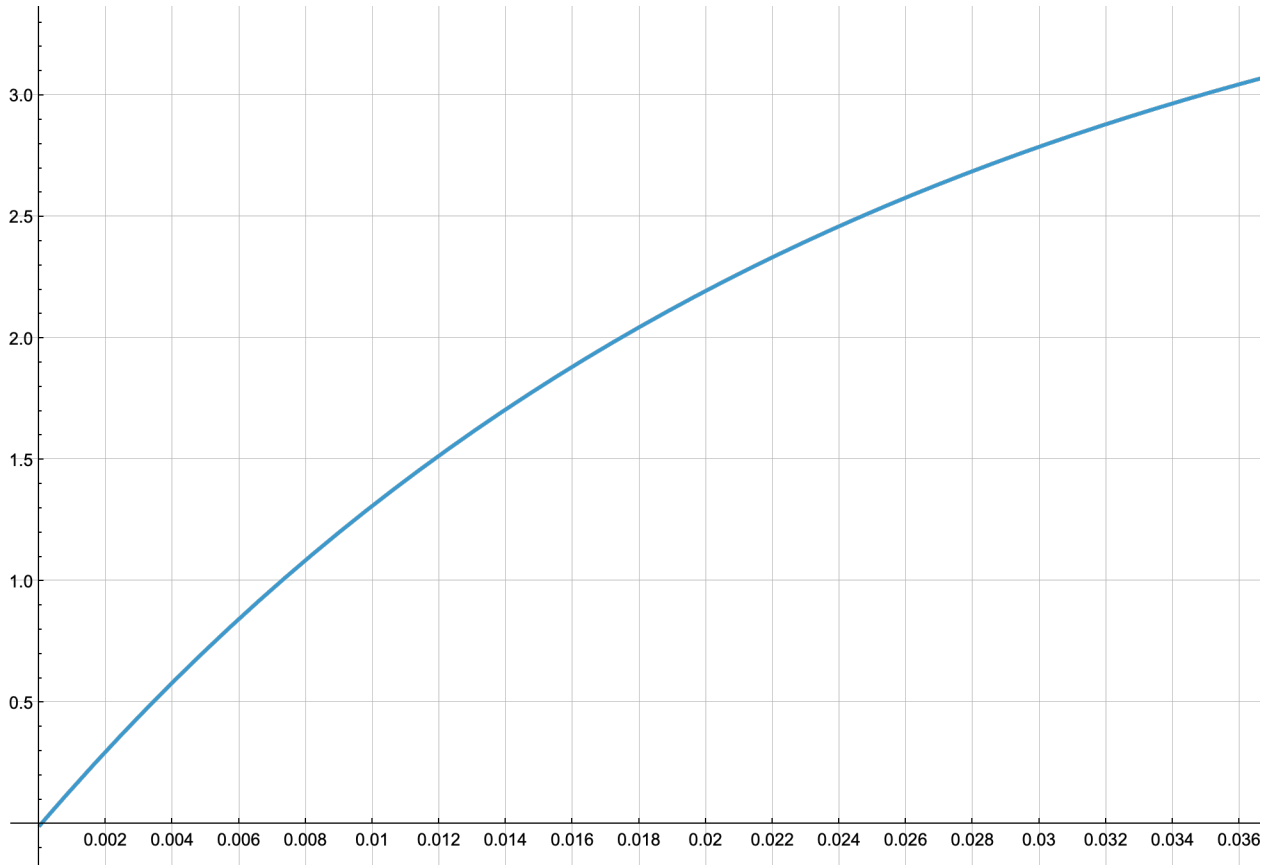

Op Amps in Non-Inverting Configuration from Victoria

3. Determining V_{in}

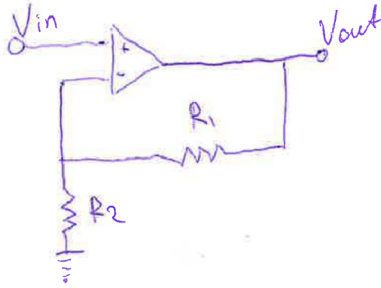

Problem 1:

$$R_2 = 500 \Omega$$

$$R_1 = 6k \Omega$$

$$V_{out} = 3V$$

- What is the value of V_{in} ?
- What can be changed in the circuit to get $V_{in} = 1.5V$?

4. Determining some possible values of R_1 and R_2


Problem 2:

$$V_{in} = 9V$$

$$V_{out} = 20V$$

- What are 3 possible combinations of R_1 and R_2 in the circuit?
- What value R_1 can never have?

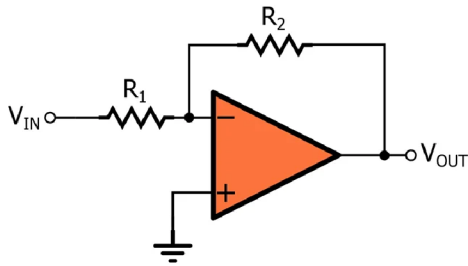Op Amps in Inverting Configuration from Nik



5. Determining V_{out}

If...

$$V_{in} = 0.5 \text{ V}$$

$$R_1 = 2 \text{ k}\Omega$$

$$R_2 = 8 \text{ k}\Omega$$

What is V_{out} ?

6. Determining V_{in}

If...

$$V_{out} = -9 \text{ V}$$

$$R_1 = 5 \text{ k}\Omega$$

$$R_2 = 15 \text{ k}\Omega$$

What is V_{in} ?

BONUS

Is it possible to solve for V using Ohm's law instead of the inverting configuration formula?

RC Low-Pass Filter from Brian

If f is the frequency of a signal, usually specified in Hz, and C is a capacitance, usually measured in microfarads, nanofarads, or picofarads, then there is a strange sense in which $\frac{1}{2\pi f C}$ can be thought of as a resistance. A capacitor is not really a resistor, but go along with it. At least this combination has the units of Ohms, like a resistor! On the next page are some problems that build on this weird idea.


7. A Strange Way of Thinking about Capacitors — High Frequencies Pass Easier Through a Capacitor than Low Frequencies

(a) If a capacitor has capacitance $C = 100$ nF (nanofarads) and a low-frequency signal with frequency $f = 50$ Hz is applied, what is the “not really a resistance” resistance of the capacitor? Call your answer R' and round to the nearest significant figure. You will use this result in 8(a).

(b) If the same capacitor has an $f = 5000$ Hz signal applied to it, what is the “not really a resistance” resistance? Call that R'' and again round to the nearest significant figure. You will use this result in 8(b).

CROSSCHECK: Your answer for (b) should be 100x smaller than your answer for (a). Notice that a capacitor’s “not really a resistance” resistance decreases as frequency increases.

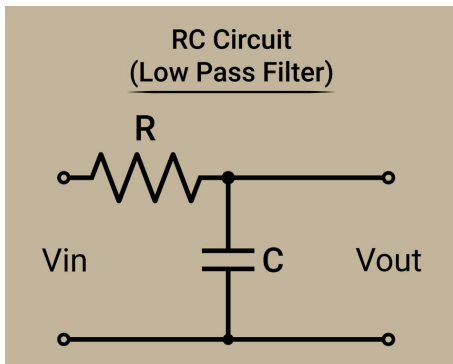8. Thinking of a Capacitor as a Resistor in a Voltage Divider



If the capacitor labeled C was actually a resistance with $R' = \frac{1}{2\pi fC}$, then in that case you should be able to see that V_{out} is in a voltage divider configuration and you'd have:

$$V_{out} = V_{in} \frac{R'}{R+R'}$$

The capacitor is not a resistor. Weirdly, the actual relation is:

$$V_{out} = V_{in} \frac{R'}{\sqrt{R^2+R'^2}}$$

(a) If $R = 3000 \Omega$, and the applied signal V_{in} has size 10V and frequency 50Hz, and using your answer for R' from 7(a) what is $V_{out} = V_{in} \frac{R'}{\sqrt{R^2+R'^2}}$?

(b) Keeping $R = 3000 \Omega$, and V_{in} having size 10V, but this time $f = 5000$ Hz, and using your answer for R'' from 7(b), what is $V_{out} = V_{in} \frac{R''}{\sqrt{R^2+R''^2}}$?